

#### INTRODUCTION

Since the introduction of second generation microprocessors, there has been a steady increase in the need for larger RAM memory for microcomputer systems. This need for larger RAM memory is due in part to the availability of higher level languages such as PL/M, PL/Z, FORTRAN, BASIC and COBOL. Until now, when faced with the need to add memory to a microcomputer system, most designers have chosen static memories such as the 2102 1Kx1 or possibly one of the new 4Kx1 static memories. However, as most mini or mainframe memory designers have learned, 16-pin dynamic memories are often the best overall choice for reliability, low power, performance, and board density. This same philosophy is true for a microcomputer system. Why then have microcomputer designers been reluctant to use dynamic memory in their system? The most important reason is that second generation microprocessors such as the 8080 and 6800 do not provide the necessary signals to easily interface dynamic memories into a microcomputer system.

Today, with the introduction of the Z80, a true third generation microprocessor, not only can a microcomputer designer increase system throughput by the use of more powerful instructions, but he can also easily interface either static or dynamic memories into the microcomputer system. This application note provides specific examples of how to interface 16-pin dynamic memories to the Z80.

#### OPERATION OF 16-PIN DYNAMIC MEMORIES

The 16-pin dynamic memory concept, pioneered by MOSTEK, uses a unique address multiplexing technique which allows memories as large as 16,384 bits x 1 to be packaged in a 16-pin package. For example the MK4027 (4,096x1 dynamic MOS RAM) and the MK4116 (16,384x1 dynamic MOS RAM) both use address multiplexing to load the address bits into memory. The MK4027 needs 12 address bits to select 1 out of 4,096 locations, while the MK4116 requires 14 bits to select 1 out of 16,384. The internal memories of the MK4027 and MK4116 can be thought of as a matrix. The MK4027 matrix can be thought of as 64x64, and the MK4116 as 128x128. To select a particular location, a row and column address is supplied to the memory. For the MK4027, address bits A<sub>0</sub>-A<sub>5</sub> are the row address, and bits A<sub>6</sub>-A<sub>11</sub>

are the column addresses. For the MK4116, address bits A<sub>0</sub>-A<sub>6</sub> are the row address, and A<sub>7</sub>-A<sub>13</sub> are the column address. The row and column addresses are strobed into the memory by two negative going clocks called Row Address Strobe ( $\overline{\text{RAS}}$ ) and Column Address Strobe ( $\overline{\text{CAS}}$ ). By the use of  $\overline{\text{RAS}}$  and  $\overline{\text{CAS}}$ , the address bits are latched into the memory for access to the desired memory location.

Dynamic memories store their data in the form of a charge on a small capacitor. In order for the dynamic memory to retain valid data, this charge must be periodically restored. The process by which data is restored in a dynamic memory is known as refreshing. A refresh cycle is performed on a row of data each time a read or write cycle is performed on any bit within the given row. A row consists of 64 locations for the MK4027 and 128 locations for the MK4116. The refresh period for the MK4027 and the MK4116 is 2ms which means that the memory will retain a row of data for 2ms without a refresh. Therefore, to refresh all rows within 2ms, a refresh cycle must be executed every 32 $\mu$ s (2ms÷64) for the MK4027 and 16 $\mu$ s (2ms÷128) for the MK4116.

To ensure that every row within a given memory is refreshed within the specified time, a refresh row address counter must be implemented either in external hardware or as an internal CPU function as in the Z80. (Discussed in more detail under Z80 Refresh Control and Timing.) The refresh row address counter should be incremented each time that a refresh cycle is executed. When a refresh is performed, all RAMs in the system should be loaded with the refresh row address. For the MK4027 and the MK4116, a refresh cycle consists of loading the refresh row address on the address lines and then generating a  $\overline{\text{RAS}}$  for all RAMs in the system. This is known as a  $\overline{\text{RAS}}$  only refresh. The row that was addressed will be refreshed in each memory. The  $\overline{\text{RAS}}$  only refresh prevents a conflict between the outputs of all the RAMs by disabling the output on the MK4116, and maintaining the output state from the previous memory cycle on the MK4027.

#### Z80 TIMING AND MEMORY CONTROL SIGNALS

The Z80 was designed to make the job of interfacing

to dynamic memories easier. One of the reasons the Z80 makes dynamic memory interfacing easier is because of the number of memory control signals that are available to the designer. The Z80 control signals associated with memory operations are:

**MEMORY REQUEST ( $\overline{MREQ}$ )** - Memory request signal indicating that the address bus holds a valid memory address for a memory read, memory write, or memory refresh cycle.

**READ ( $\overline{RD}$ )** - Read signal indicating that the CPU wants to read data from memory or an I/O device. The addressed I/O device or memory should use this signal to gate data onto the CPU data bus.

**WRITE ( $\overline{WR}$ )** - Write signal indicating that the CPU data bus hold valid data to be stored in the addressed memory or I/O device.

**REFRESH ( $\overline{RFSH}$ )** - Refresh signal indicates that the lower 7 bits of the address bus contain a refresh address for dynamic memories and the current  $\overline{MREQ}$  signal should be used to generate a refresh cycle for all dynamic memories in the system.

Figures 1a, 1b, and 1c show the timing relationships of the control signals, address bus, data bus and system clock  $\Phi$ . By using these timing diagrams, a set of equations can be derived to show the worst case access times needed for dynamic memories with the Z80 operating at 2.5MHz.

The access time needed for the op code fetch cycle and the memory read cycle can be computed by equations 1 and 2.

$$(1) t_{\text{ACCESS OP CODE}} = 3(t_c/2) \cdot t_{DL\overline{\Phi}(MR)} \cdot t_{S\overline{\Phi}(D)}$$

where:  $t_c$  = Clock period

$t_{DL\overline{\Phi}(MR)}$  =  $\overline{MREQ}$  delay from falling edge of clock.

$t_{S\overline{\Phi}(D)}$  = Data setup time to rising edge of clock during op code fetch cycle.

let:  $t_c = 400\text{ns}$ ;  $t_{DL\overline{\Phi}(MR)} = 100\text{ns}$ ;  $t_{S\overline{\Phi}} = 50\text{ns}$

then:  $t_{\text{ACCESS OP CODE}} = 450\text{ns}$

$$(2) t_{\text{ACCESS MEMORY READ}} = 4(t_c/2) \cdot t_{DL\overline{\Phi}(MR)} \cdot t_{S\overline{\Phi}(D)}$$

where:  $t_c$  = Clock period

$t_{DL\overline{\Phi}(MR)}$  =  $\overline{MREQ}$  delay from falling edge of clock

$t_{S\overline{\Phi}(D)}$  = Data Setup time to falling edge of clock

let:  $t_c = 400\text{ns}$ ;  $t_{DL(MR)} = 100\text{ns}$ ;  $t_{S(D)} \overline{\Phi} = 60\text{ns}$

then:  $t_{\text{ACCESS MEMORY READ}} = 640\text{ns}$

The access times computed in equations 1 and 2 are overall worst case access times required by the CPU. The overall access times must include all TTL buffer delays and the access time for the memory device. For example, a typical dynamic memory design would have the following characteristics, (see Figure 2).


The example in Figure 2 shows an overall access time of 336ns. This would more than satisfy the 450ns required for the op code fetch and the 640ns required for a memory read.

CPU  $\overline{MREQ}$  buffer delay . . . . . 12ns (8T97)  
Memory gating and timing delays . . . . . 40ns  
Memory device access time . . . . . 250ns (MK4027/4116-4)  
Memory data bus buffer delay . . . . . 17ns (8T28)  
CPU data bus buffer delay . . . . . 17ns (8T28)

336ns


## OP CODE FETCH TIMING

Figure 1a.

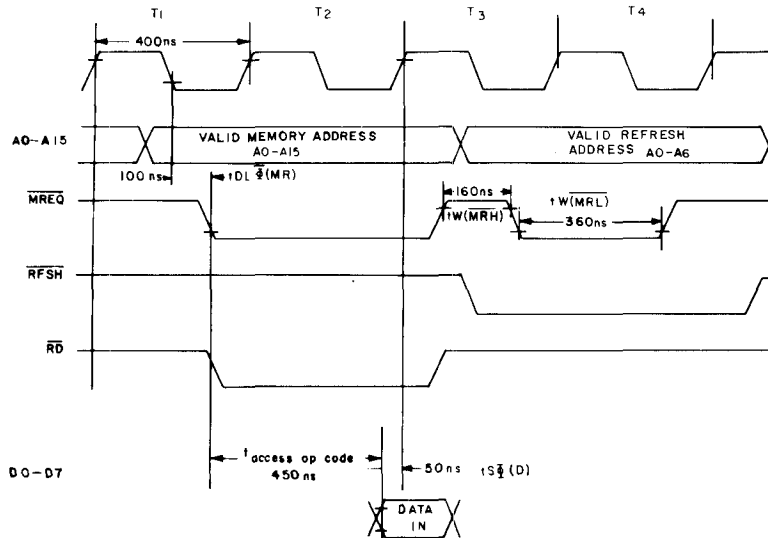

## MEMORY READ TIMING


Figure 1b.

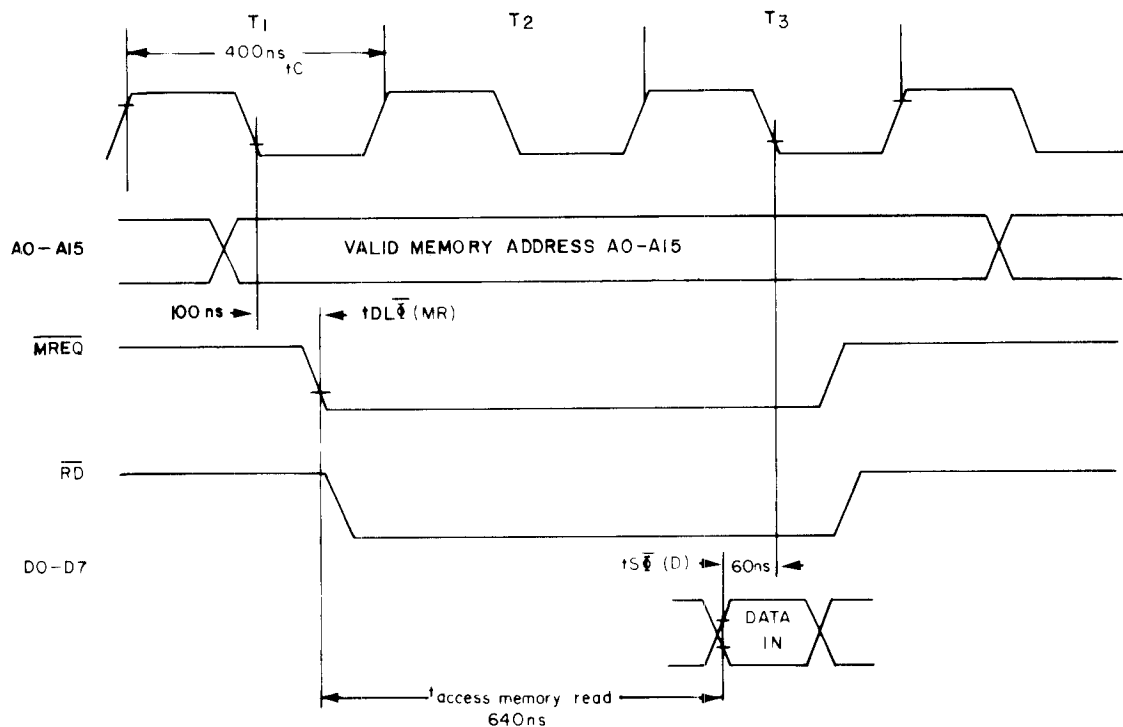

DYNAMIC  
RAMS

## MEMORY WRITE TIMING

Figure 1c.

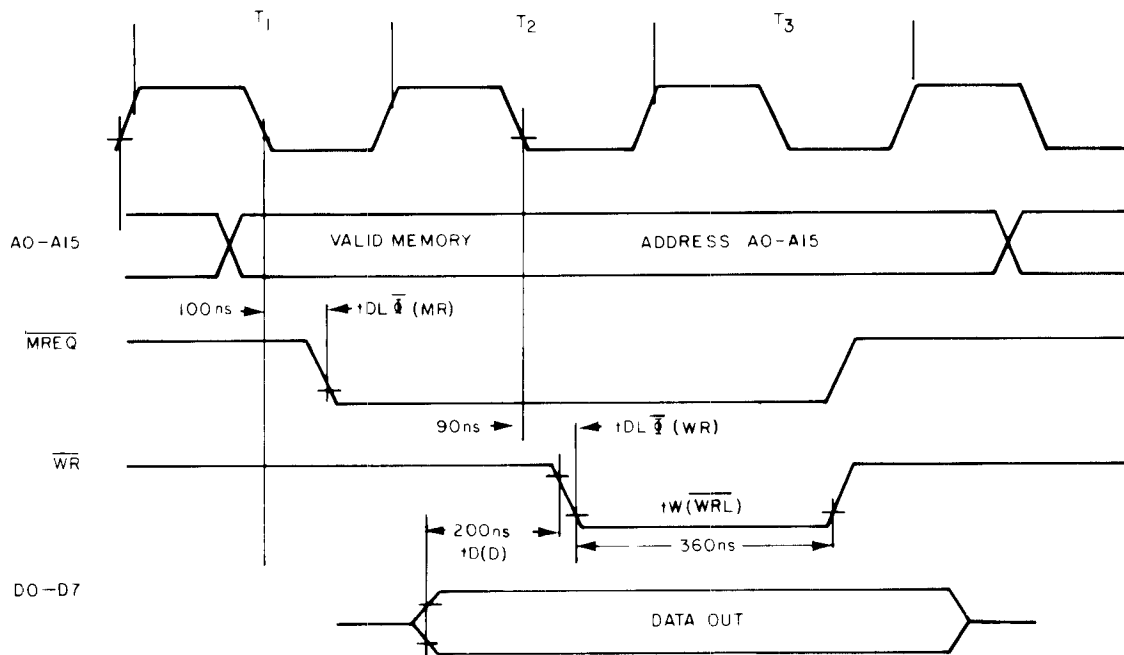

## Z80 REFRESH CONTROL AND TIMING

One of the most important features provided by the Z80 for interfacing to dynamic memories is the execution of a refresh cycle every time an op code fetch cycle is performed. By placing the refresh cycle in the op code fetch, the Z80 does not have to allocate time in the form of "wait states" or by "stretching" the clock to perform the refresh cycle. In other words, the refresh cycle is "totally transparent" to the CPU and does not decrease the system throughput (see Figure 1a). The refresh cycle is transparent to the CPU because, once the op code has been fetched from memory during states  $T_1$  and  $T_2$ , the memory would normally be idle during states  $T_3$  and  $T_4$ .

Therefore, by placing the refresh in the  $T_3$  and  $T_4$  states of the op code fetch, no time is lost for refreshing dynamic memory. The critical timing parameters involving the Z80 and dynamic memories during the refresh cycle are:  $t_W(MRH)$  and  $t_W(MRL)$ . The parameter known as  $t_W(MRH)$  refers to the time that  $\overline{MREQ}$  is high during the op code fetch between the fetch of the op code and the refresh cycle. This time is known as "precharge" for dynamic memories and is necessary to allow certain internal nodes of the RAM to be charged-up for another memory cycle. The equation for the minimum  $t_W(MRH)$  time period is:

$$(3) \quad t_W(MRH) = t_W(\Phi H) + t_f - 30$$

where:  $t_W(\Phi H)$  is clock pulse width high  
 $t_f$  is clock fall time

let:  $t_W(\Phi H) = 180\text{ns}$ ;  $t_f = 10\text{ns}$

then:  $t_W(MRH) = 160\text{ns (min)}$

A  $t_W(MRH)$  of 160ns is more than adequate to meet the worst case precharge times for most dynamic RAMs. For example, the MK4027-4 and the MK4116-4 require a 120ns precharge. The other refresh cycle parameter of importance to dynamic RAMs is  $t_W(MRL)$ , (the time that  $\overline{MREQ}$  is low during the refresh cycle). This time is important because  $\overline{MREQ}$  is used to directly generate  $\overline{RAS}$ . The equation for the minimum time period is:

$$(4) \quad t_W(MRL) = t_c - 40$$

where:  $t_c$  is the clock period

let:  $t_c = 400\text{ns}$

then:  $t_W(MRL) = 360\text{ns}$

A 360ns  $t_W(MRL)$  exceeds the 250ns min  $\overline{RAS}$  time required for the MK4027-4 and the MK4116-4.

By controlling the refresh internally with the Z80, the designer must be aware of one limitation. The limitation is that to refresh memory properly, the Z80 CPU must be able to execute op codes since the refresh cycle occurs during the op code fetch. The following conditions cause the execution of op codes to be inhibited, and will destroy the contents of dynamic memory.


- (1) Prolonged reset  $> 1\text{ms}$
- (2) Prolonged wait state operation  $> 1\text{ms}$
- (3) Prolonged bus acknowledge (DMA)  $> 1\text{ms}$
- (4)  $\Phi$  clock of  $< 1.216\text{ MHz}$  for 16K RAMs  
 $< .608\text{ MHz}$  for 4K RAMs

The clocks rate in number 4 are based on the Z80 continually executing the worst case instruction which is an EX (SP), HL that executes in 19 T states. Therefore, by operating the Z80 at or above these clocks frequencies, the user is ensured that the dynamic memories in the system will be refreshed properly.

Remember to refresh memory properly, the Z80 must be able to execute op codes!

## DELAY FOR A TYPICAL MEMORY SYSTEM

Figure 2.

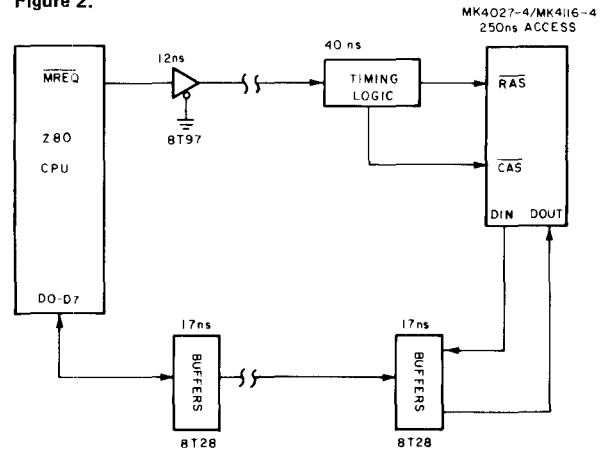

## SUPPORT CIRCUITS FOR DYNAMIC MEMORY INTERFACE


Two support circuits are necessary to ensure reliable operation of dynamic memory with the Z80.

The first of these circuits is an address latch shown in Figure 3. The latch is used to hold addresses  $A_{12}$ - $A_{15}$  while  $\overline{MREQ}$  is active. This action is necessary because the Z80 does not ensure the validity of the address bus at the end of the op code fetch (see Figure 4). This action does not directly affect dynamic memories because they latch addresses internally. The problem comes from the address decoder which generates  $\overline{RAS}$ . If the address lines which drive the decoder are allowed to change while  $\overline{MREQ}$  is low, then a "glitch" can occur on the  $\overline{RAS}$  line or lines (if more than one row of RAMs are used) which may have the effect of destroying one row of data.

The second support circuit is used to generate a power on and short manual reset pulse. Recall from the discussion under Z80 Timing and Memory Con-

## ADDRESS LATCH


Figure 3.

 

DYNAMIC  
RAMS

## RAS TIMING WITH AND WITHOUT ADDRESS LATCH

Figure 4.

 


ontrol Signals that one of the conditions that will cause dynamic memory to be destroyed is a reset pulse of duration greater than 1ms. The circuit shown in Figure 5a can be used to generate a short reset pulse from either a push button or an external source. Additionally the manual reset is synchronized to the start of an M1 cycle so that the reset will not fall during the middle of a memory cycle. Along with

the manual reset, the circuit will also generate a power on reset.

If it is not necessary that the contents of the dynamic memory be preserved, then the reset circuit shown in Figure 5b may be used to generate a manual or power on reset.


#### MANUAL AND POWER-ON RESET CIRCUIT

Figure 5a.

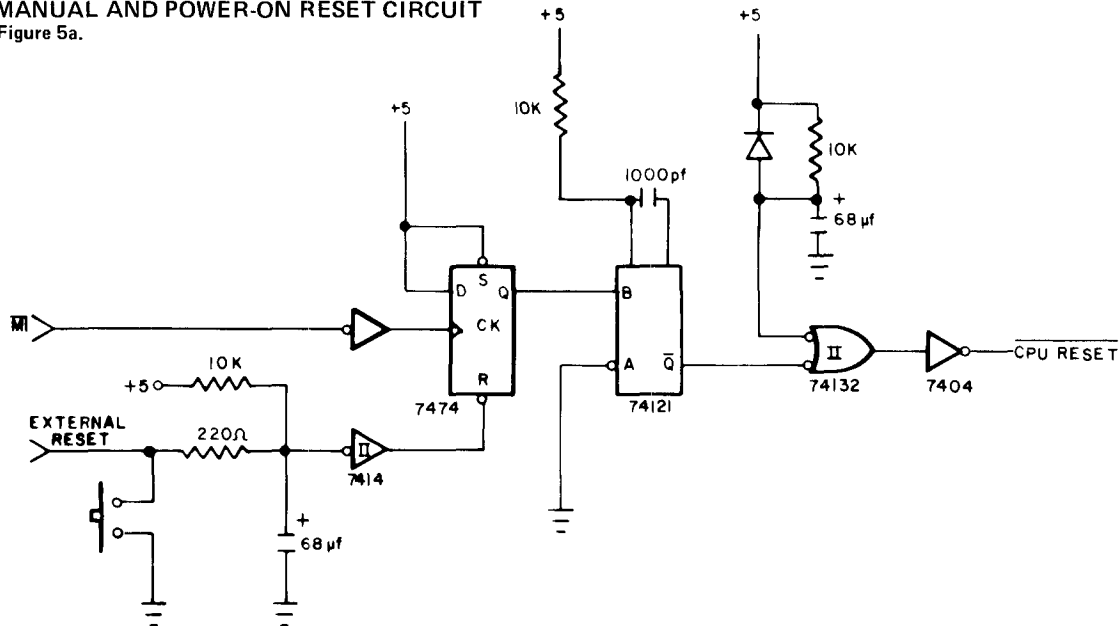


#### MANUAL AND POWER-ON RESET CIRCUIT

Figure 5b.

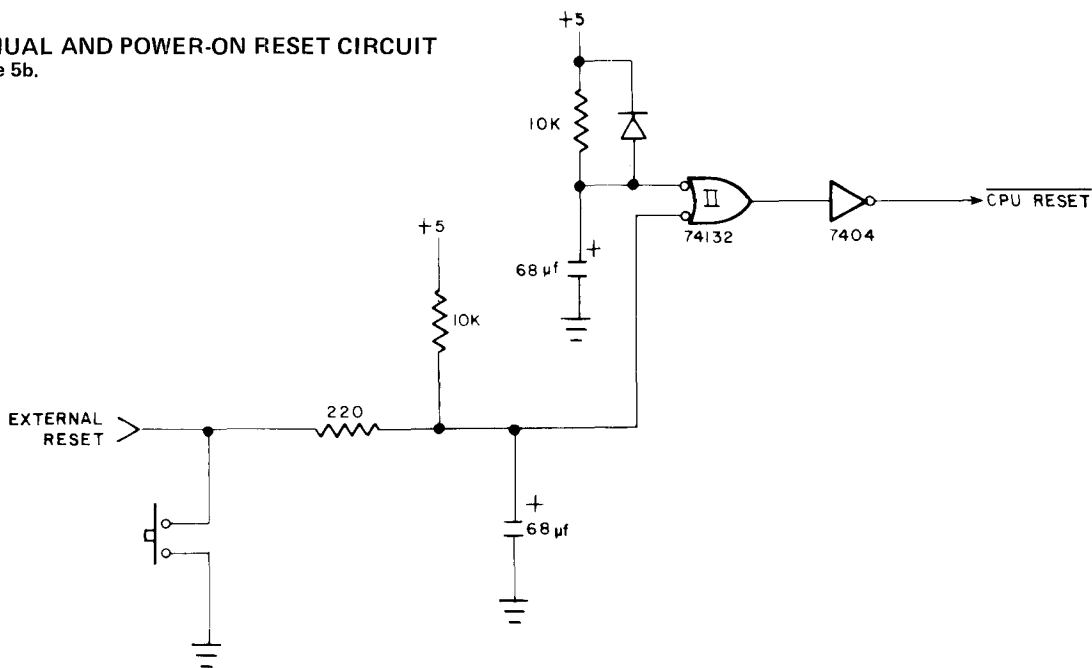

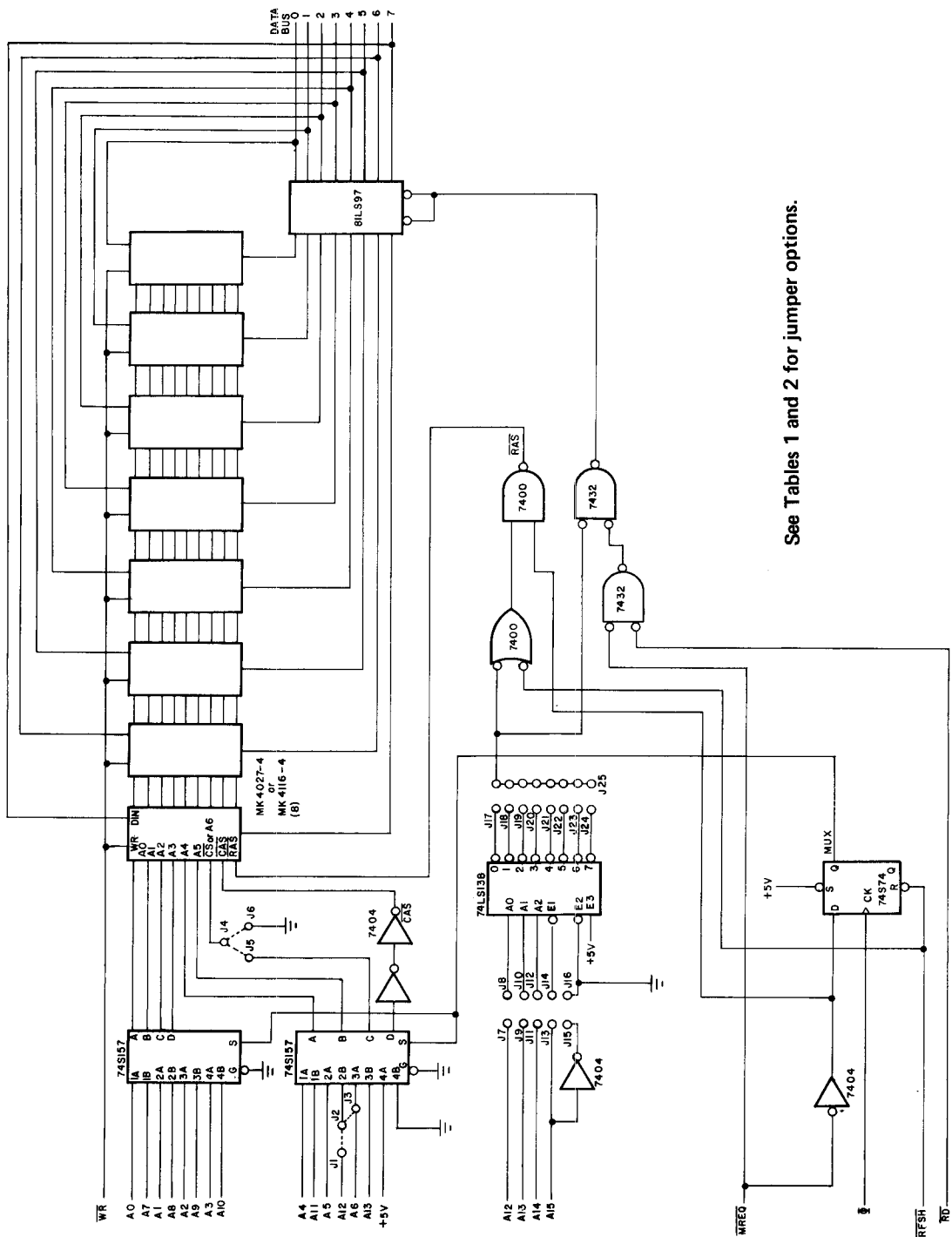DESIGN EXAMPLE NO. 1 SCHEMATIC DIAGRAM  
Figure 6.



See Tables 1 and 2 for jumper options.

DYNAMIC  
RAMS

## DESIGN EXAMPLES FOR INTERFACING THE Z80 TO DYNAMIC MEMORY

To illustrate the interface between the Z80 and dynamic memory, two design examples are presented. Example number 1 is for a 4K/16Kx8 memory and the example number 2 is a 16K/64Kx8 memory.

### Design Example Number 1: 4K/16Kx8 Memory

This design example describes a 4K/16Kx8 memory that is best suited for a small single board Z80 based microcomputer system. The memory devices used in the example are the MK4027 (4,096x1 MOS Dynamic RAM) and the MK4116 (16,384x1 MOS Dynamic RAM). A very important feature of this design is the ease in which the memory can be expanded from a 4Kx8 to a 16Kx8 memory. This is made possible by the use of jumper options which configure the memory for either the MK4027 or the MK4116. See Table 1 and 2 for jumper options.


Figure 6 shows the schematic diagram for the 4K/16Kx8 memory. A timing diagram for the Z80 control signals and memory control signals is shown in Figure 7. The operation of the circuit may be described as follows:  $\overline{RAS}$  is generated by NANDing  $\overline{MREQ}$  with  $\overline{RFSH} + \text{ADDRESS DECODE}$ .  $\overline{RFSH}$  is generated directly from the Z80 while address decode comes from the 74LS138 decoder. Address decode indicates that the address on the bus falls within the memory boundaries of the memory. If an op code fetch or memory read is being executed the 81LS97 output buffer will be enabled at approximately the same time as  $\overline{RAS}$  is generated for the memory array. The output buffer is enabled only

during an op code fetch or memory read when  $\overline{\text{ADDRESS DECODE}}$ ,  $\overline{MREQ}$ , and  $\overline{RD}$  are all low. The switch multiplexer signal (MUX) is generated on the rising edge of  $\Phi$  after  $\overline{MREQ}$  has gone low during an op code fetch, memory read or memory write. After MUX is generated and the address multiplexers switch from the row address to column address,  $\overline{CAS}$  will be generated.  $\overline{CAS}$  comes from one of the outputs of the multiplexer and is delayed by two gate delays to ensure that the proper column address set-up time will be achieved. Once  $\overline{RAS}$  and  $\overline{CAS}$  have been generated for the memory array, the memory will then access the desired location for a read or write operation.

7404	22ns	} Generate $\overline{RAS}$ from $\overline{MREQ}$
7400	15ns	
	63ns	$\overline{RAS}$ to rising edge of $\Phi$
74S74	10ns	$\Phi$ to MUX
74S157	15ns	} Generate $\overline{CAS}$ from MUX
7404	22ns	
7404	15ns	
$t_{CAC}$	165ns	$\overline{CAS}$ access time
81LS97	22ns	Output buffer delay
	349ns	Worst case access

### DESIGN EXAMPLE NO. 1 MEMORY TIMING

Figure 7.

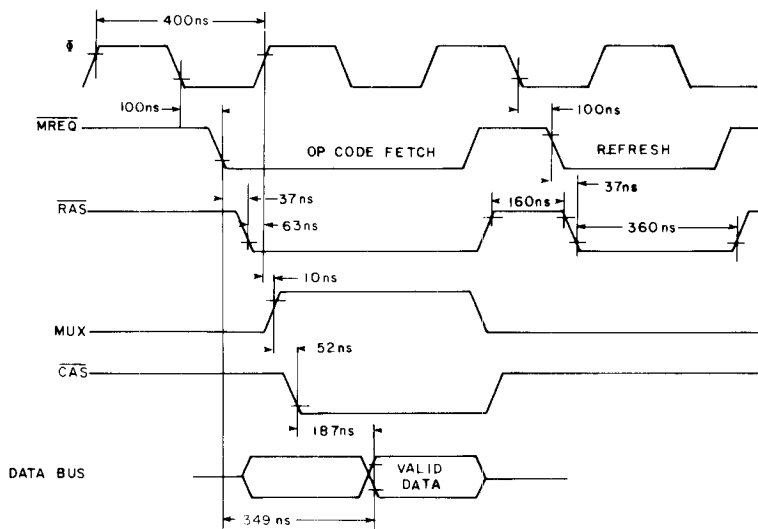



The worst case access time required by the CPU for the op code fetch is 450ns (from equation 1); therefore, the circuit exceeds the required access time by 101ns (worst case).

The circuit shown in Figure 6 provides excellent performance when used as a small on board memory. The memory size should be held at eight devices because there is not sufficient timing margin to allow the interface circuit to drive a larger memory array.

## Design Example Number 2: 16Kx8 Memory

This design example describes a 16K/64Kx8 memory which is best suited for a Z80 based microcomputer system where a large amount of RAM is desired. The memory devices used in this example are the same as for the first example, the MK4027 and the MK4116. Again as with the first example, the memory may be expanded from a 16Kx8 to a 64Kx8 by reconfiguring jumpers. See Table 3 and 4 for jumper options.

Figure 8 shows the schematic diagram for the 16K/64K memory. A timing diagram is shown in Figure 9. The operation of the circuit can be described as follows:  $\overline{RAS}$  is generated by NANDing MREQ with ADDRESS DECODE (from the two 74LS138s) + RFSH. Only one row of RAMs will receive a  $\overline{RAS}$  during an op code fetch, memory read or memory write. However, a  $\overline{RAS}$  will be generated for all rows within the array during a refresh cycle.  $\overline{MREQ}$  is inverted and fed into a TTL compatible delay line to generate MUX and  $\overline{CAS}$ . (This particular approach differs from the method used in example number 1 in that all memory timing is referenced to MREQ, whereas the circuit in example number 1 bases its

memory timing from both  $\overline{MREQ}$  and the clock. Both methods offer good results, however, the TTL delay line approach offers the best control over the memory timing.) MUX is generated 65ns later and is used to switch the 74157 multiplexers from the row to the column address. The 65ns delay was chosen to allow adequate margin for the row address hold time  $t_{RAH}$ . At 110ns,  $\overline{CAS}$  is generated from the delay line and NANDed with RFSH, which inhibits a  $\overline{CAS}$  during refresh cycle. After  $\overline{CAS}$  is applied to the memory, the desired location is then accessed. A worst case access timing analysis for the circuit shown in Figure 8 can be computed as follows:

74LS14	22ns	}	Generate $\overline{RAS}$ from $\overline{MREQ}$
74LS00	15ns		
delay line	50ns	}	MUX from $\overline{RAS}$
delay line	45ns		
7400	20ns	}	$\overline{CAS}$ delay from MUX
$t_{CAC}$	165ns		
8833	30ns		Access time from $\overline{CAS}$
			Output buffer delay
	347ns		

DYNAMIC RAMS

The required access time from the CPU is 450ns (from equation 1). This leaves 103ns of margin for additional CPU buffers on the control and address lines. This particular circuit offers excellent results for an application which requires a large amount of RAM memory. As mentioned earlier, the memory timing used in this example offers the best control over the memory timing and would be ideally suited for an application which required direct memory access (DMA).

## 4K x 8 CONFIGURATION (MK4027) JUMPER

Table 1

CONNECT: J13 to J14		Connect: J2 to J3		CONNECT: J14 to J15	
ADDRESS	CONNECT	J4 to J6		ADDRESS	CONNECT
0000-0FFF	J17 to J25	J7 to J8		8000-8FFF	J17 to J25
1000-1FFF	J18 to J25	J9 to J10		9000-9FFF	J18 to J25
2000-2FFF	J19 to J25	J11 to J12		A000-AFFF	J19 to J25
3000-3FFF	J20 to J25			B000-BFFF	J20 to J25
4000-4FFF	J21 to J25			C000-CFFF	J21 to J25
5000-5FFF	J22 to J25			D000-DFFF	J22 to J25
6000-6FFF	J23 to J25			E000-EFFF	J23 to J25
7000-7FFF	J24 to J25			F000-FFFF	J24 to J25

## 16K x 8 CONFIGURATION (MK4116) JUMPER CONNECTIONS

Table 2

CONNECT:	J1 to J2	ADDRESS	CONNECT
	J4 to J5		
	J8 to J11	0-3FFF	J17 to J25
	J10 to J13	4000-7FFF	J18 to J25
	J12 to J16	8000-BFFF	J19 to J25
	J14 to J16	C000-FFFF	J20 to J25

---

**16K x 8 CONFIGURATION (MK4027)****Table 3**

CONNECT: J1 to J3  
J5 to J6  
J7 to J8  
J9 to J10  
J11 to J12  
J13 to J14

ADDRESS: 0-3FFF	ADDRESS: 4000-7FFF	ADDRESS: 8000-BFFF	ADDRESS: C000-FFFF
CONNECT: J24 to J25	CONNECT: J16 to J17	CONNECT: J40 to J41	CONNECT: J32 to J33
J26 to J27	J18 to J19	J42 to J43	J34 to J35
J28 to J29	J20 to J21	J44 to J43	J36 to J37
J30 to J31	J22 to J23	J46 to J47	J38 to J39

---

**64K x 8 CONFIGURATION (MK4116)****Table 4**

CONNECT: J1 to J2	ADDRESS: 0-FFFF
J4 to J5	CONNECT: J32 to J33
J8 to J11	J34 to J35
J10 to J13	J36 to J37
J12 to J15	J38 to J39
J14 to J15	

---

**SYSTEM PERFORMANCE CHARACTERISTICS****Table 5**


The system characteristics for the preceeding design examples are shown in Table 5.

EXAMPLE #	MEMORY CAPACITY	MEMORY ACCESS	POWER REQUIREMENTS
1	4K/16Kx8	349ns max.	+12V @ 0.0250 A max. +5V @ 0.422 A max. * -5V @ 0.030 A max.
2	16K/64Kx8	347ns max.	+12V @ 0.600 A max. +5V @ 0.550 A max. * -5V @ 0.030 A max.

\*All power requirements are max.; operating temperature 0°C to 70°C ambient, max +12V current computed with Z80 executing continuous op code fetch cycles from RAM at 1.6  $\mu$ s intervals.

# DESIGN EXAMPLE NO. 2 SCHEMATIC DIAGRAM

Figure 8.

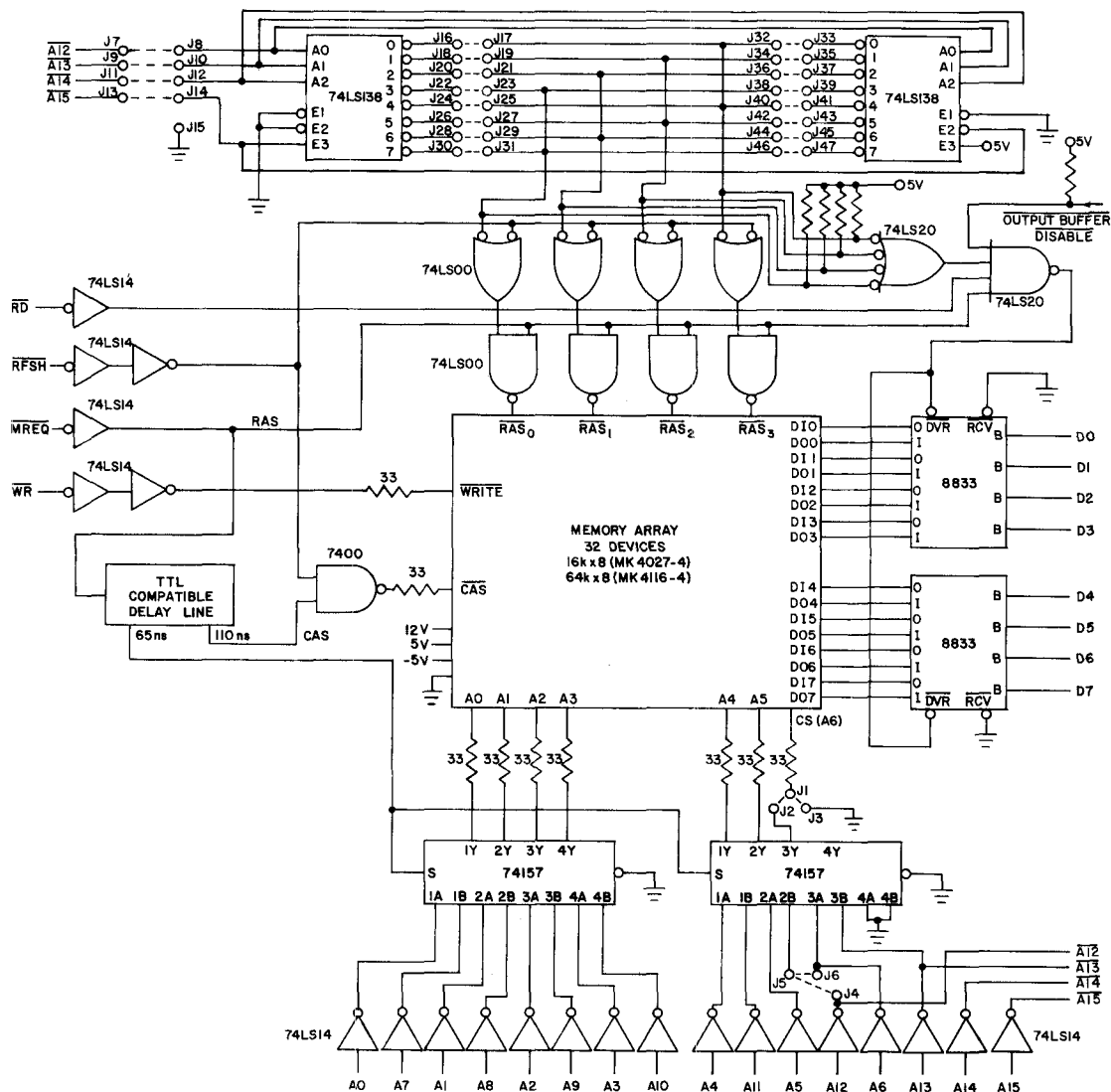


DYNAMIC  
RAMS

FOR JUMPER OPTIONS SEE TABLES 3 AND 4

## DESIGN EXAMPLE NO. 2 MEMORY TIMING

Figure 9.

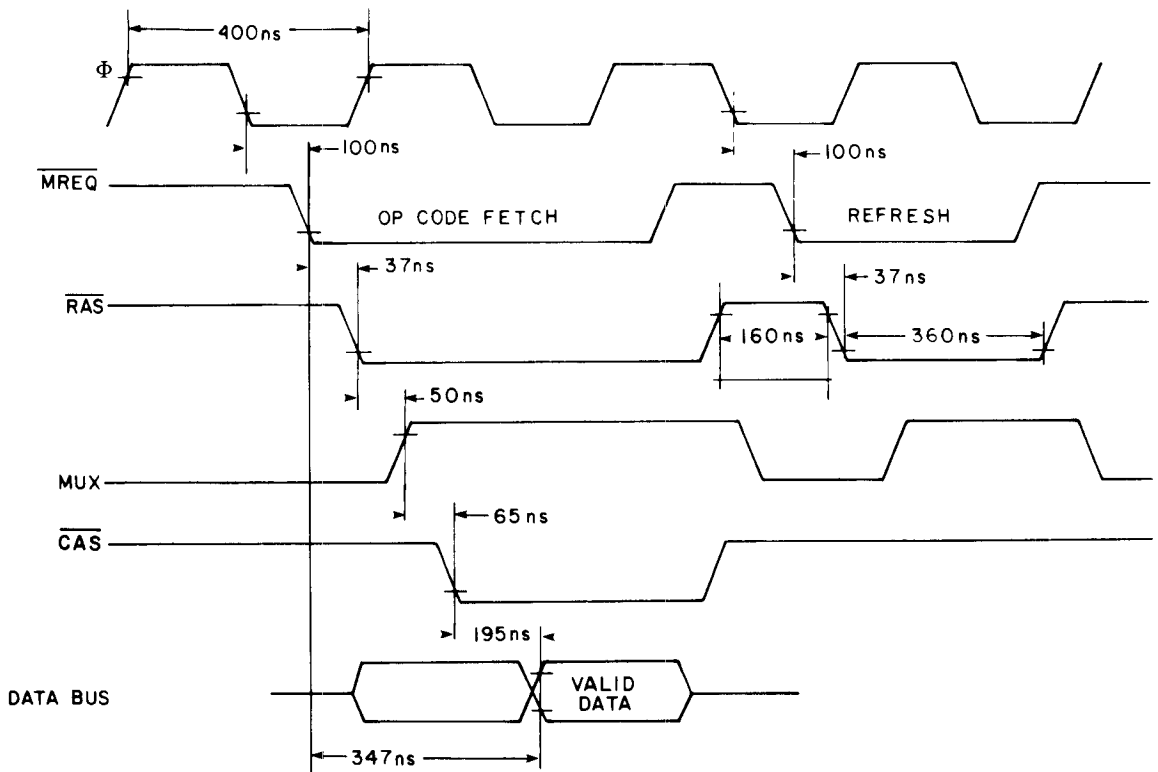

## PRINTED CIRCUIT LAYOUT

One of the most important parts of a dynamic memory design is the printed circuit layout. Figure 10 illustrates a recommended layout for 32 devices. A very important factor in the P.C. layout is the power distribution. Proper power distribution on the  $V_{DD}$  and  $V_{BB}$  supply lines is necessary because of the transient current characteristics which dynamic memories exhibit. To achieve proper power distribution,  $V_{DD}$ ,  $V_{BB}$ ,  $V_{CC}$  and ground should be laid out in a grid to help minimize the power distribution impedance. Along with good power distribution, adequate capacitive bypassing for each device in the memory array is necessary. In addition to the individual by-passing capacitors, it is recommended that each supply ( $V_{BB}$ ,  $V_{CC}$  and  $V_{DD}$ ) be bypassed with an electrolytic capacitor 20 $\mu$ F.

By using good power distribution techniques and using the recommended number of bypassing capacitors, the designer can minimize the amount of noise in the memory array. Other layout considerations


are the placement of signal lines. Lines such as address, chip select, column address strobe, and write should be bussed together as rows; then, bus all rows together at one end of the array. Interconnection between rows should be avoided. Row address strobe lines should be bussed together as a row, then connected to the appropriate  $\overline{RAS}$  driver. TTL drivers for the memory array signals should be located as close as possible to the array to help minimize signal noise.

For a large memory array such as the one shown in design example number 2, series terminating resistors should be used to minimize the amount of negative undershoot. These resistors should be used on the address lines,  $\overline{CAS}$  and  $\overline{WRITE}$ , and have values between 20  $\Omega$  to a 33  $\Omega$ .

The layout for a 32 device array can be put in a 5" x 5" area on a two sided printed circuit board.

SUGGESTED P. C. LAYOUT FOR MK4027 or MK4116

Figure 10.

 

DYNAMIC  
RAMS

## 4MHz Z80 DYNAMIC MEMORY INTERFACE CONSIDERATIONS

A 4MHz Z80 is available for the microcomputer designer who needs higher system throughput. Considerations which must be faced by the designer when interfacing the 4MHz Z80 to dynamic memory are the need for memories with faster access times and for providing minimum RAM precharge time. The access times required for dynamic memory interfaced to a 4MHz Z80 can be computed from equations 1 and 2 under Z80 Timing and Memory Control Signals.

Access time for op code fetch for 4MHz Z80,  
 let:  $t_C = 250\text{ns}$ ;  $t_{D\overline{\Phi}}(MR) = 75\text{ns}$ ;  $t_{s\overline{\Phi}}(D) = 35\text{ns}$   
 then:  $t_{\text{ACCESS OP CODE}} = 265\text{ns}$   
 Access time for memory read for 4MHz Z80,  
 let:  $t_C = 250\text{ns}$ ;  $t_{D\overline{\Phi}}(MR) = 75\text{ns}$ ;  $t_{s\overline{\Phi}}(D) = 50\text{ns}$   
 then:  $t_{\text{ACCESS MEMORY READ}} = 375\text{ns}$

The problem of faster access times can be solved by using 200ns memories such as the MK4027-3 or MK4116-3. Depending on the number of buffer delays in the system, the designer may have to use 150ns memories such as the MK4027-2 or MK4116-2. The most critical problem that exists when interfacing dynamic memory to the 4MHz Z80 is the RAM precharge time (trp). This parameter is called  $t_{W(MRH)}$  on the Z80 and can be computed by the following equation.

$$(4) \quad t_{W(MRH)} = t_{W(\Phi H)} + t_f - 20\text{ns}$$

let:  $t_{W(\Phi H)} = 110\text{ns}$ ;  $t_f = 5\text{ns}$   
 then:  $t_{W(MRH)} = 95\text{ns}$


A  $t_{W(MRH)}$  of 95ns will not meet the minimum precharge time of the MK4027-2 or MK4116-2 which is 100ns. The MK4027-3 and MK4116-3 require a 120ns precharge. Figure 11 shows a circuit that will lengthen the  $t_{W(MRH)}$  pulse from 95ns to a minimum of 126ns while only inserting one gate delay into the access timing chain. Figure 12 shows the timing for the circuit of Figure 11. The operation of the circuit in Figure 11 can be explained as follows: The D flip flops are held in a reset condition until MREQ goes to its active state. After MREQ goes active, on the next positive clock edge, the D input of U1 and U2 will be transferred to the outputs of the flip flops. Output QA will go high if M1 was high when  $\Phi$  clocked U1. Output QB will go low on the next positive going clock edge, which will cause the output of U3 to go low and force the output of U4, which is  $\overline{\text{RAS}}$ , high. The flip flops will be reset when MREQ goes inactive.

The circuit shown in Figure 11 will give a minimum of 126ns precharge for dynamic memories, with the Z80 operating at 4MHz. The 126ns  $t_{W(MRH)}$  is computed as follows.

110ns	$t_{W(\Phi H)}$ - clock pulse width high (min)
5ns	$t_f$ - clock full time (min)
20ns	$t_{D\overline{\Phi}}(MR)$ - MREQ delay (min)
-9ns	74S74 delay (min)
126ns	$t_{W(MRH)}$ modified (min)


## 4MHz Z80 PRECHARGE EXTENDER FOR DYNAMIC MEMORIES

Figure 11

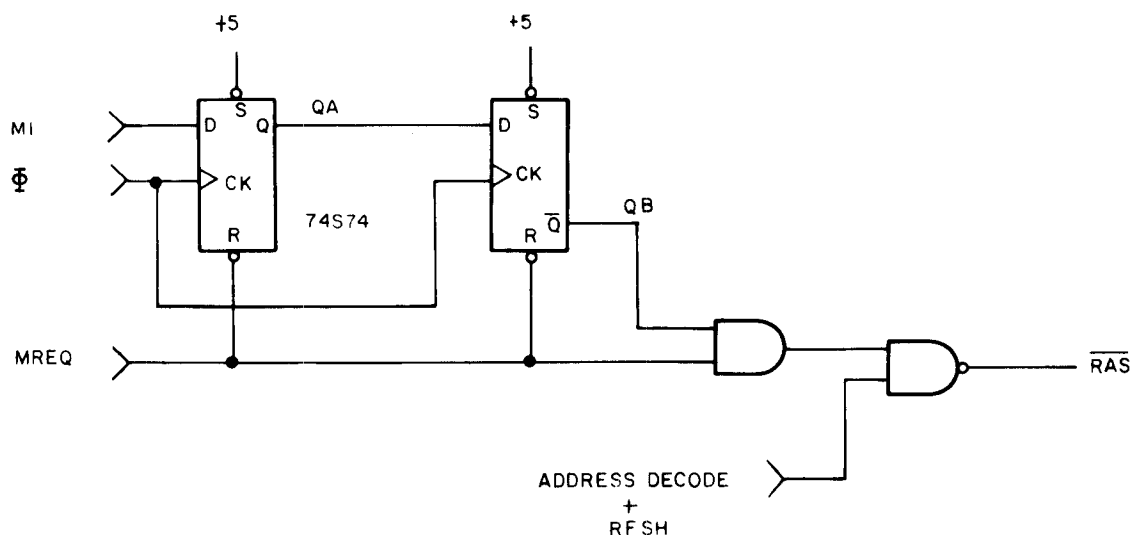

# TIMING DIAGRAM FOR 4MHz Z80 PRECHARGE EXTENDER

Figure 12

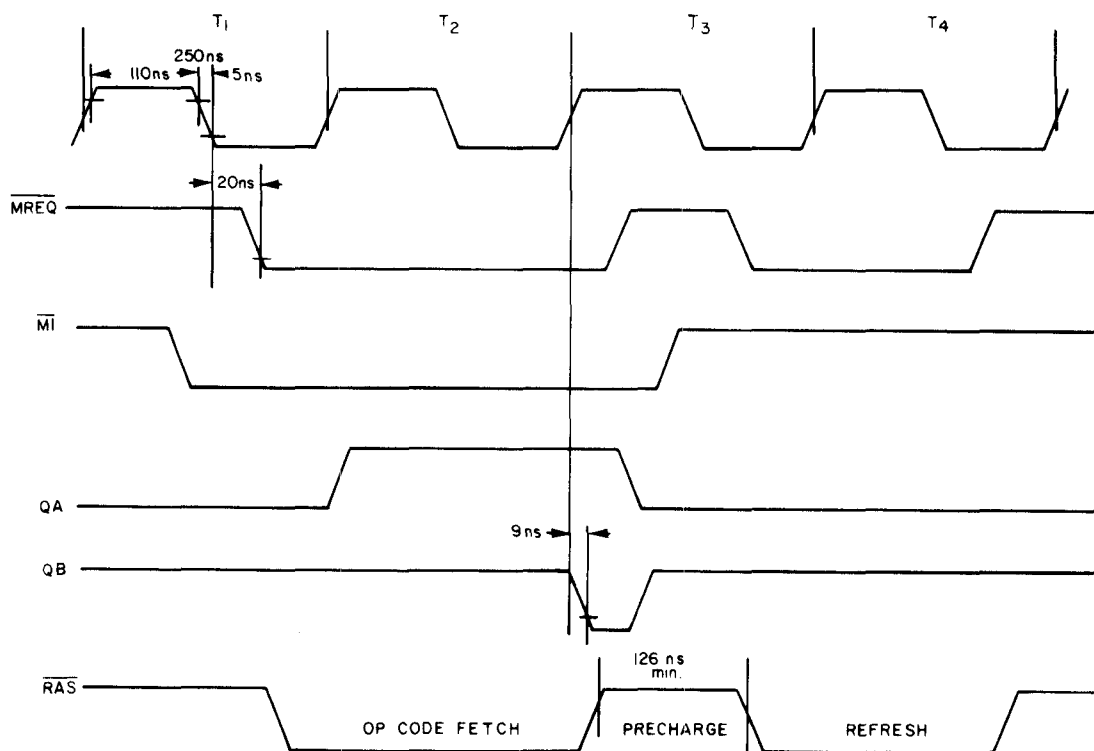

DYNAMIC RAMS

## APPENDIX

### MEMORY TEST ROUTINE

This section is intended to give the microcomputer designer a memory diagnostic suitable for testing memory systems such as the ones shown in Section VI.

The routine is a modified address storage test with an incrementing pattern. A complete test requires 256<sub>10</sub>

passes, which will execute in less than 4 minutes for a 16Kx8 memory. If an error occurs, the program will store the pattern in location '2C'H and the address of the error at locations '2D'H and '2E'H.

The program is set up to test memory starting at location '2F'H up to the end of the block of memory defined by the bytes located at '0C'H and '0D'H. The test may be set up to start at any location by modifying locations '03'H - '04'H and '11'H - '12'H with the starting address that is desired.

LOC	OBJ CODE	STMT SOURCE STATEMENT	MXRTS LISTING	PAGE	0001
0001		;TRANSLATED FROM DEC 1976 INTERFACE MAGAZINE			
0002		;			
0003		;THIS IS A MODIFIED ADDRESS STORAGE TEST WITH AN			
0004		;INCREMENTING PATTERN			
0005		;			
0006		;256 PASSES MUST BE EXECUTED BEFORE THE MEMORY IS			
0007		;COMPLETELY TESTED.			
0008		;			
0009		;IF AN ERROR OCCURS, THE PATTERN WILL BE STORED			
0010		;AT LOCATION '002C'H AND THE ADDRESS OF THE			
0011		;ERROR LOCATION WILL BE STORED AT '002D'H AND			
0012		;'002E'H.			
0013		;			

# MEMORY TEST ROUTINE (Cont'd.)

```

0014 ;THE CONTENTS OF LOCATIONS '000C'H AND '001D'H
0015 ;SHOULD BE SELECTED ACCORDING TO THE FOLLOWING
0016 ;MEMORY SIZE TO BE TESTED
0017 ;
0018 ;TOP OF MEMORY TO
0019 ;BE TESTED
0020 ;
0021 ;      4K
0022 ;      8K
0023 ;     16K
0024 ;     32K
0025 ;     48K
0026 ;     64K
0027 ;
0028 ;THE PROGRAM IS SET UP TO START TESTING AT
0029 ;LOCATION '002F'H. THE STARTING ADDRESS FOR THE
0030 ;TEST CAN BE MODIFIED BY CHANGING LOCATIONS
0031 ;'0003-0004'H AND '0011-0012'H.
0032 ;
0033 ;TEST TIME FOR A 16K X 8 MEMORY IS APPROX. 4 MIN
0034 ;
0000      0000      0035      ORG      0000H
0000      0600      0036      LD      B,0          ;CLEAR B PATRN MODIFIER
0002      212F00    0037 ;LOAD UP MEMORY
0005      7D        0038 LOOP:    LD      HL,START  ;GET STARTING ADDR
0006      AC        0039 FILL:    LD      A,L        ;LOW BYTE TO ACCM
0007      A8        0040          XOR      E          ;XOR WITH HIGH BYTE
0008      77        0041          XOR      B          ;XOR WITH PATTERN
0009      23        0042          LD      (HL),A      ;STORE IN ADDR
000A      7C        0043          INC      HL         ;INCREMENT ADDR
000B      FE10      0044          LD      A,H         ;LOAD HIGH BYTE OF ADDR
000D      C20500    0045          CP      EPAGE       ;COMPARE WITH STOP ADDR
0010      212F00    0046          JP      NZ,FILL     ;NOT DONE,GO BACK
0013      7D        0047 ;READ AND CHECK TEST DATE
0014      AC        0048          LD      HL,START  ;GET STARTING ADDR
0015      A8        0049 TEST:    LD      A,L        ;LOAD LOW BYTE
0016      BE        0050          XOR      H          ;XOR WITH HIGH BYTE
0017      C22500    0051          XOR      B          ;XOR WITH MODIFIER
001A      23        0052          CP      (HL)        ;COMPARE WITH MEMORY LOC
001B      7C        0053          JP      NZ,FXIT     ;ERROR EXIT
001C      FE10      0054          INC      HL         ;UPDATE MEMORY ADDRESS
001E      C21300    0055          LD      A,H         ;LOAD HIGH BYTE
0021      04        0056          CP      EPAGE       ;COMPARE WITH STOP ADDR
0022      04        0057          JP      NZ,TEST     ;LOOP BACK
0023      04        0058          INC      B          ;UPDATE MODIFIER

```

LOC	OBJ CODE	STMT	SOURCE STATEMENT	PAGE	0002
0022	C30200	0059	JP LOOP		
		0060	;ERROR EXIT		
0025	222D00	0061	LD (BYTE),HL		
0028	322C00	0062	LD (PATRN),A		
002B	76	0063	HALT		
002C		0064	PATRN: DEFS 1		
002D		0065	BYTE: DEFS 2		
002F	2F00	0066	START: DEFW S		
		0068	EPAGE: EQU 10H		
		0069	END		